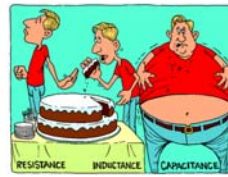




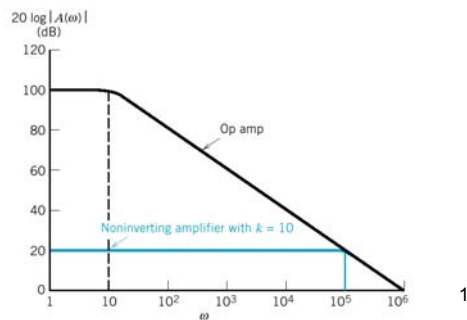
# Frequency response



- Static analysis
  - Low frequency response
  - Response without capacitive effect
- Real circuit response
  - Strongly dependant on frequency
  - Small signal analysis with (major) capacitances (and inductors for RF)

- Typical operational amplifier response
  - Gain strongly dependent on frequency
- Frequency response
  - Important performance measure
  - Gain-Bandwidth





1



# Frequency response

- Gain changing with signal frequency

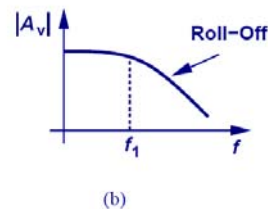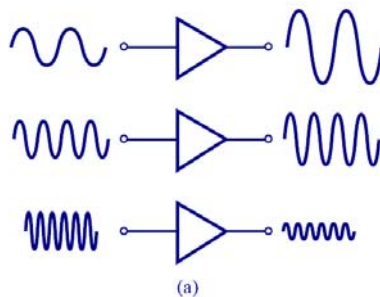


- Sinusoidals may be combined to construct any signal

2



# Simple low-pass filter

- Passive filter

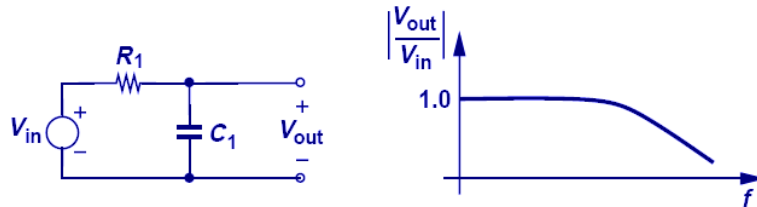

- $C_1$ 
  - high impedance a low frequency
  - Reduced impedance with increasing frequency


TSL inf3410

3




# CS stage with load

- Finding transfer function

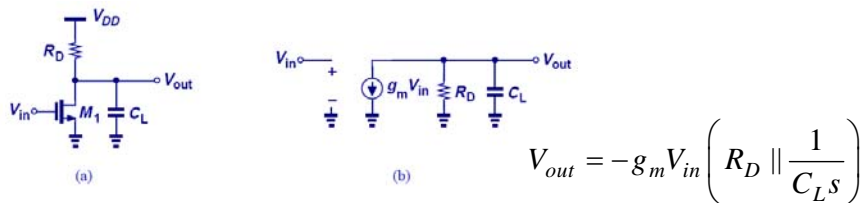

- Simply by adding capacitance impedance to output load

- magnitude

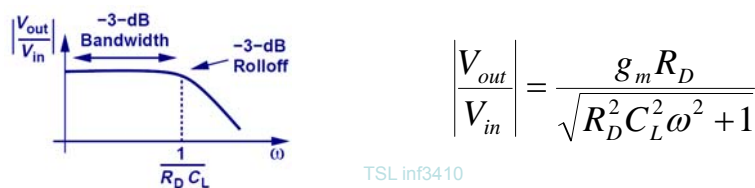


TSL inf3410

4



# Bandwidth

- Example

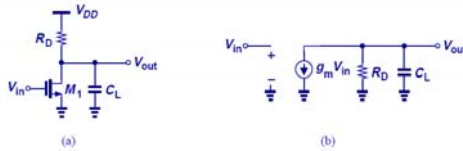


$$H(s) = \frac{V_{out}}{V_{in}}(s) = -g_m (R_D \parallel \frac{1}{C_L s})$$

$$= \frac{-g_m R_D}{R_D C_L s + 1}$$

$$s = j\omega \rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{R_D^2 C_L^2 \omega^2 + 1}}$$

$$\omega = 1/(R_D C_L) \left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{2}}$$

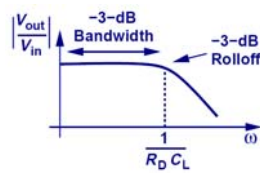

Time constant or -3dB bandwidth

TSL inf3410


5


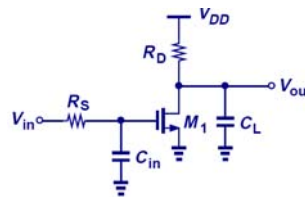
# Nodes and poles

- Poles are often associated to nodes

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \dots}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \dots}$$



$$\left| \omega_{p1} \right| = \frac{1}{R_S C_{in}} \quad \left| \omega_{p2} \right| = \frac{1}{R_D C_L}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{\left(1 + \omega^2 / \omega_{p1}^2\right) \left(1 + \omega^2 / \omega_{p2}^2\right)}}$$


TSL inf3410

6



# What about this?

- CS stage with feedback

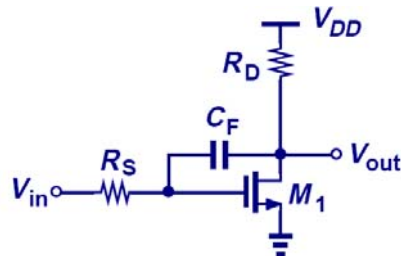


- Nodes connected by floating capacitor
- Simple node for each pole does not work
- Must transform before analysis
  - Caps to ground.....

TSL inf3410


7



# Miller Theorem

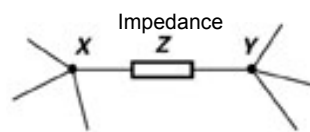

(a)

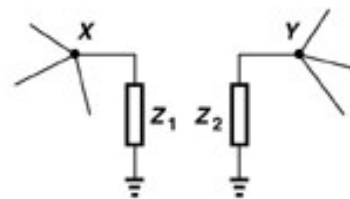

(b)

- If circuit (a) is converted to (b) then:

$$Z_1 = \frac{Z}{1 - A_v} \quad Z_2 = \frac{Z}{\left(1 - \frac{1}{A_v}\right)} \quad A_v = \frac{V_y}{V_x}$$


*Approximation!*

8



## Example

- Ideal amp with feedback capacitor

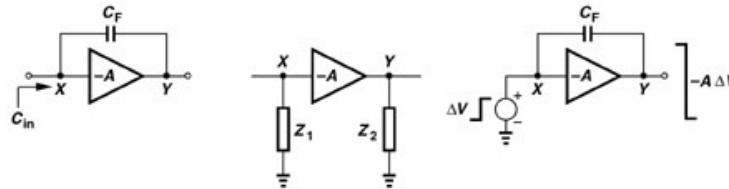

$$Z = 1/sC_F \Rightarrow Z_1 = (1/sC_F)/(1+A)$$

$$\Rightarrow C_1 = C_F(1+A)$$

$$Z = 1/sC_F \Rightarrow Z_2 = (1/sC_F)/(1+1/A)$$

$$\Rightarrow C_2 = C_F(1+A^{-1}) \approx C_F$$

TSL inf3410

9

## Simple 1. order filter



- Passive


$$V_o/V_i = \frac{1/sC}{R+1/sC}$$

$$V_o/V_i = \frac{1}{sRC+1}$$

$$\frac{V_o}{V_i}(f) = \frac{1}{1+(j2\pi f)RC}$$

$$\frac{V_o}{V_i}(f) = \frac{1}{1+jf/f_p}, \quad f_p = 1/2\pi RC$$

TSL inf3410

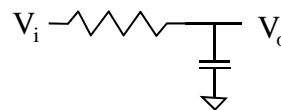


10



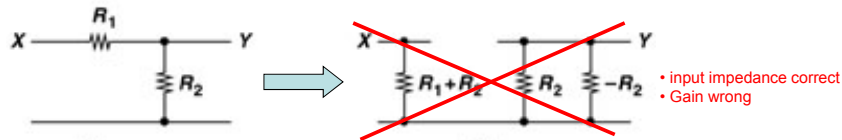
## Limited usage

- Do not work for passive voltage divider



- Typical case for Miller theorem

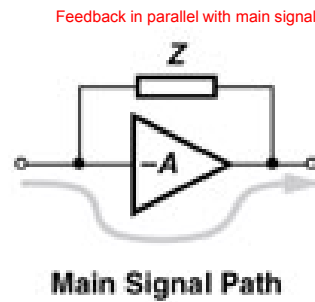


TSL inf3410

11



## Example

- Determine input impedance using Miller

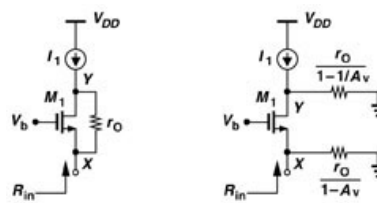

$$\begin{aligned}
 R_{in} &= \frac{r_o}{1 - [1 + (g_m + g_{mb})r_o]} \parallel \frac{1}{g_m + g_{mb}} \\
 &= \frac{-1}{g_m + g_{mb}} \parallel \frac{1}{g_m + g_{mb}} \\
 &= \infty
 \end{aligned}$$

Determined in chapter 3 as well


TSL inf3410

12



## Poles and nodes

- Assuming one pole for each node

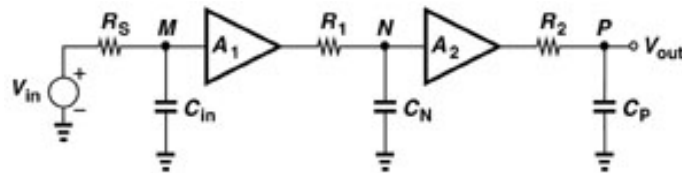

- Total gain by multiplying each stage gain

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_S C_{in}} \cdot \frac{A_2}{1 + sR_1 C_N} \cdot \frac{1}{1 + sR_2 C_P}$$

*Simple and easy 1. order approximation*


TSL inf3410

13



## Example

- Determine pole at node X

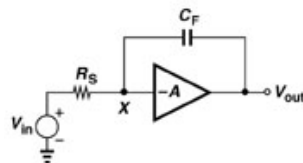

- Using Miller to find input impedance to ground:

$$Z_1 = (1 + A)C_F$$

- Time-constant by multiplying by  $R_S$

$$f_{p-in} = \frac{1}{2\pi(R_S \cdot (1 + A)C_F)} \quad / \text{ Hz}$$

TSL inf3410

14



## Example

- More complicated to appreciate nodal analysis
  - Neglecting channel length modulation

$$f_{p-in(X)} = \frac{1}{2\pi \left[ (C_{GS} + C_{SB}) \left( R_S \parallel \left( \frac{1}{g_m + g_{mb}} \right) \right) \right]}$$

$$f_{p-out(Y)} = \frac{1}{2\pi \left[ (C_{GD} + C_{DB}) R_D \right]}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \cdot \frac{1}{(1 + s/2\pi f_{p-in(X)}) \cdot (1 + s/2\pi f_{p-out(Y)})}$$

With channel length modulation, things are hard due to input-output interaction

15



## Analysis procedure

1. Determine capacitors affecting low-frequency response
2. Calculate mid-band gain by shorting these caps
3. Identify and add transistors capacitors
4. Note AC ground and try to get rid of caps not affecting performance
5. Determine high frequency poles and zeros
6. Plot frequency response or find equation


TSL inf3410

16



# Low frequency response

- CS stage

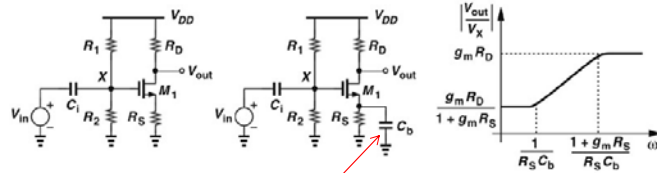

– Transfer function:

$$V_{out}/V_{in} = (V_{out}/V_X)(V_X/V_{in})$$

$$V_{out}/V_X = -R_D/(R_S + 1/g_m)$$

$$\frac{V_X}{V_{in}}(s) = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + \frac{1}{C_i s}}$$

$$= \frac{(R_1 \parallel R_2) C_i s}{(R_1 \parallel R_2) C_i s + 1}$$

– High pass filter on input

- Cut-off below lowest signal frequency

$$\frac{1}{2\pi[(R_1 \parallel R_2) C_i]} < f_{sig, min}$$

– Bypass capacitor

- Removing degeneration for mid-band frequencies

$$\frac{V_{out}}{V_X}(s) = \frac{-R_D}{R_S \parallel \frac{1}{C_b s} + \frac{1}{g_m}} = \frac{-g_m R_D (R_S C_b s + 1)}{R_S C_b s + g_m R_S + 1}$$


TSL inf3410

17



# High frequency MOS model

- Adding transistor capacitances

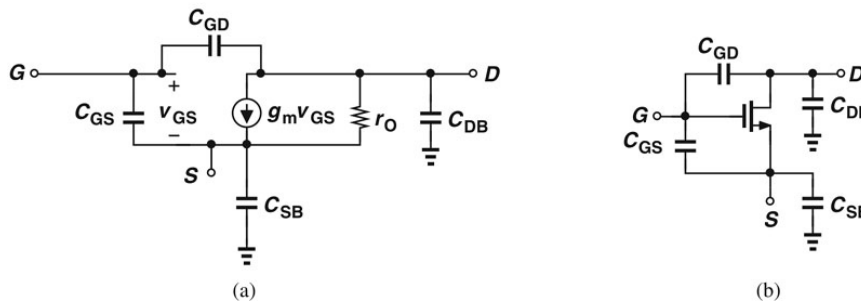

- $C_{GD}$  appear as a floating or coupling capacitance
- Other caps decoupling
  - Except when source is not ground connected

TSL inf3410

18



# High frequency response

- Using Millers theorem
  - Ignoring channel length modulation

$$C_X = (1 + g_m R_L) C_{XY}$$

$$C_Y = \left(1 + \frac{1}{g_m R_L}\right) C_{XY}$$


- Poles at each node

$$|\omega_{p,in}| = \frac{1}{R_{Thev} [C_{in} + (1 + g_m R_L) C_{XY}]}$$

$$|\omega_{p,out}| = \frac{1}{R_L \left[ C_{out} + \left(1 + \frac{1}{g_m R_L}\right) C_{XY} \right]} \approx \frac{1}{R_L (C_{out} + C_{XY})} \quad g_m R_L \gg 1$$

$$\frac{V_{out}}{V_{in}}(s) = \underbrace{-g_m R_D}_{\text{LF gain}} \frac{1}{(1 + s/\omega_{p,in}) \cdot (1 + s/\omega_{p,out})}$$

TSL inf3410

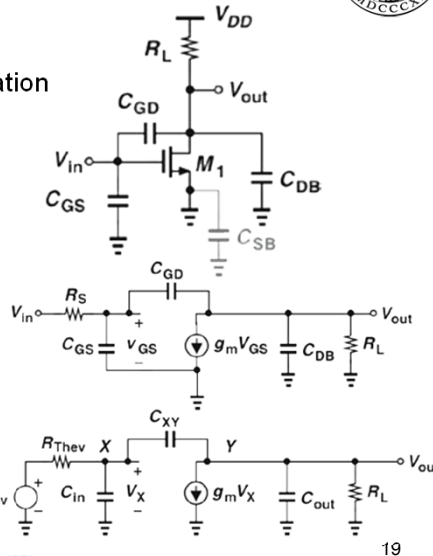


19
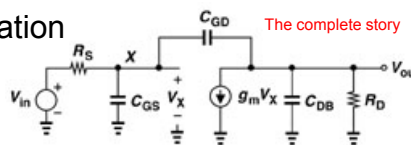
# CS small signal analysis



- Dominant pole approximation
  - Using KCL



The complete story

– Node X:  $\frac{V_X - V_{in}}{R_s} + V_X C_{GS} s + (V_X - V_{out}) C_{GD} s = 0$

– Node  $V_{out}$ :  $(V_{out} - V_X) C_{GD} s + g_m V_X + V_{out} (1/R_D + C_{DB} s) = 0 \Rightarrow$

– Insert: 
$$V_X = - \frac{V_{out} \left( s C_{GD} + \frac{1}{R_D} + s C_{DB} \right)}{g_m - s C_{GD}}$$

$$-V_{out} \frac{[R_s^{-1} + (C_{GS} + C_{GD})s][R_D^{-1} + (C_{GD} + C_{DB})s]}{g_m - C_{GD}s} - V_{out} C_{GD}s = \frac{V_{in}}{R_s}$$

TSL inf3410

20



# CS small signal analysis

- Giving transfer function:

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{s^2(R_S R_D \xi) + s[R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})] + 1}$$

- With  $\xi = C_{GD} \cdot C_{GS} + C_{GS} \cdot C_{DB} + C_{GD} \cdot C_{GB}$

- Assuming two poles (dominant pole approximation)

$$D = \left( \frac{s}{\omega_{p1}} + 1 \right) \left( \frac{s}{\omega_{p2}} + 1 \right) = \frac{s^2}{\omega_{p1} \omega_{p2}} + \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1 \quad (\omega_{p1} \ll \omega_{p2})$$

$$\omega_{p1} = \frac{1}{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$$

$$\omega_{p,in} = \frac{1}{R_S [C_{GS} + (1 + g_m R_D)C_{GD}]} \quad \leftarrow \text{Addition compared to simple Miller analysis. This is correct with good pole separation}$$

TSL inf3410

21



# CS small signal analysis

- Determining second pole

- Given  $s^2$  coefficient is  $\frac{1}{(\omega_{p1} \omega_{p2})} \Rightarrow \omega_{p2} = \frac{1}{\omega_{p1}} \frac{1}{R_S R_D \xi}$


$$\omega_{p2} = \frac{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}{R_S R_D (C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

Miller approximation

Assuming:  $C_{GS} \gg (1 + g_m R_D)C_{GD} + R_D(C_{GD} + C_{DB})/R_S \Rightarrow \omega_{p2} = \omega_{p,out} \approx \frac{1}{(C_{GD} + C_{DB})R_D}$

- Zero at  $\omega_z = +g_m / C_{GD}$

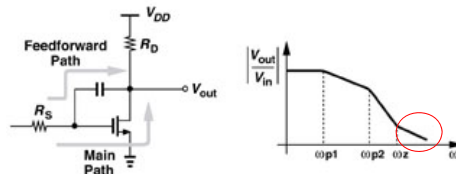
- Feed forward at high frequencies
  - Not so steep transition band
- Not predicted by Miller
- May introduce instability
  - With feedback



TSL inf3410



# Comparison of approximations

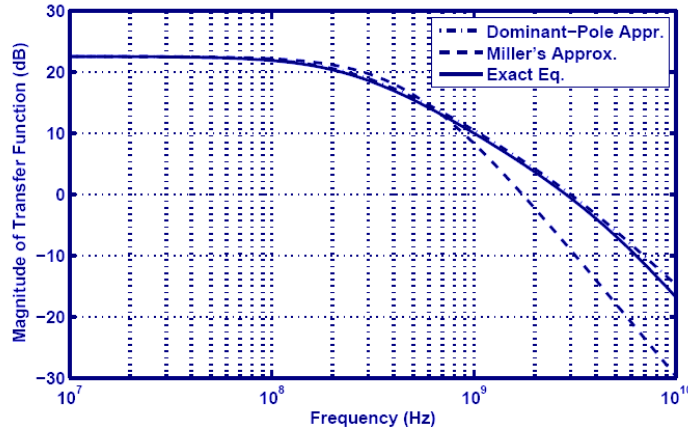

- Dominant pole approximation is reasonably good
- Miller approximation have significant errors at higher frequencies


TSL inf3410

23



# CS input impedance

- HF input impedance

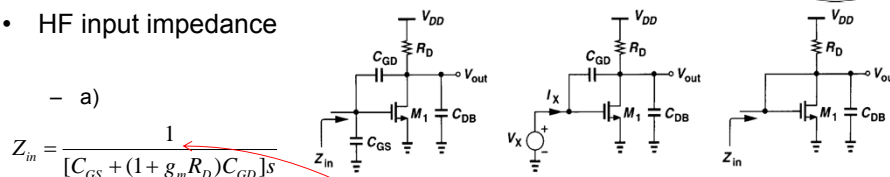

a)

$$Z_{in} = \frac{1}{[C_{GS} + (1 + g_m R_D) C_{GD}]s}$$

- b) compensating for output node variations ( $C_{GS}$  ignored)

$$V_X = (I_X - g_m V_X) \frac{R_D}{1 + R_D C_{GB} s} + \frac{I_X}{C_{GD} s}$$

Voltage change over  $C_{GD}$

Voltage change at output perturbations

$$\frac{V_X}{I_X} = \frac{1 + R_D (C_{GD} + C_{GB}) s}{C_{GD} s (1 + g_m R_D + R_D C_{GB} s)}$$

Total input impedance  $C_{GS}$  must be added in parallel

When  $R_D (C_{GD} + C_{GB}) s \ll 1$  and  $R_D C_{GB} s \ll 1 + g_m R_D$  reduce to simple form  
Load mostly capacitive!


TSL inf3410

24



# Source followers freq

- Level shifters and buffers

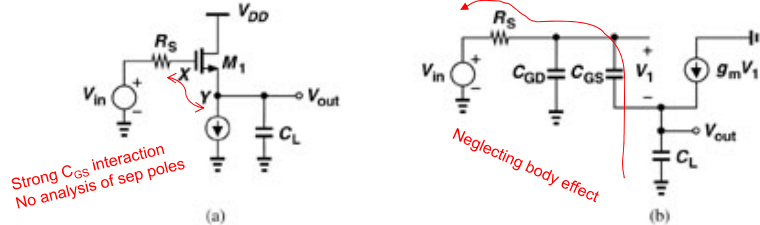

– Summing currents

$$V_1 C_{GS} s + g_m V_1 = V_{out} C_L s \Rightarrow V_1 = \frac{C_L s}{g_m + C_{GS} s} V_{out} \quad \text{KCL}$$

$$V_{in} = R_S [V_1 C_{GS} s + (V_1 + V_{out}) C_{GD} s] + V_1 + V_{out} \quad \text{KVL}$$

$$\frac{V_{out}(s)}{V_{in}} = \frac{g_m + s C_{GS}}{s^2 R_S (C_{GS} C_L + C_{GS} C_{GD} + C_{GD} C_L) + s(g_m R_S C_{GD} + C_L + C_{GS}) + g_m} \quad \text{combining}$$

TSL inf3410

25



# Follower instability

- Zero in left half-plane

$$\frac{V_{out}(s)}{V_{in}} = \frac{g_m + s C_{GS}}{s^2 R_S (C_{GS} C_L + C_{GS} C_{GD} + C_{GD} C_L) + s(g_m R_S C_{GD} + C_L + C_{GS}) + g_m}$$


- Assuming separated poles

– Dominating pole

$$f_{p1} \approx \frac{g_m}{2\pi(g_m R_S C_{GD} + C_L + C_{GS})}, \text{ assuming } f_{p2} \gg f_{p1}$$

$$= \frac{1}{2\pi \left( R_S C_{GD} + \frac{C_L + C_{GS}}{g_m} \right)}$$
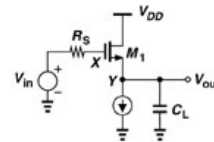
$$R_S = 0 \rightarrow f_{p1} \approx \frac{g_m}{2\pi(C_L + C_{GS})}$$



TSL inf3410

26



## Source follower input impedance

- Ignoring  $C_{GD}$

$$V_X = \frac{I_X}{sC_{GS}} + \left( I_X + \frac{g_m I_X}{sC_{GS}} \right) \left( \frac{1}{g_{mb}} \parallel \frac{1}{sC_L} \right)$$

- Assuming  $g_{mb} \gg |sC_L|$

$$Z_{in} = \frac{1}{sC_{GS}} + \left( 1 + \frac{g_m}{sC_{GS}} \right) \frac{1}{g_{mb} + sC_L}$$


$$Z_{in} \approx \frac{1}{sC_{GS}} \left( 1 + g_m / g_{mb} \right) + 1 / g_{mb}$$

- Indicating input capacitance:  $C_{in} = C_{GS} [g_{mb} / (g_m + g_{mb})] + C_{GD}$

- At HF:  $g_{mb} \ll |sC_L|$

$$Z_{in} = \frac{1}{sC_{GS}} + \left( 1 + \frac{g_m}{sC_{GS}} \right) \frac{1}{g_{mb} + sC_L} \rightarrow Z_{in} \approx \frac{1}{sC_{GS}} + \frac{1}{sC_L} + \frac{g_m}{s^2 C_{GS} C_L}$$

Negative resistance for oscillators

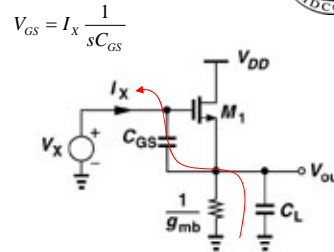

27



## Source follower output impedance

- Ignoring body effect and  $C_{GD}$

$$V_1 C_{GS} s + g_m V_1 = -I_X$$

$$(V_1 C_{GS} s) R_S + V_1 + V_X = 0$$



- Giving  $Z_{OUT} = V_X / I_X$

$$Z_{OUT} = \frac{s R_S C_{GS} + 1}{g_m + s C_{GS}}$$


- Magnitude function of frequency!

- With  $1/g_m < R_S$  for low output impedance (buffer)

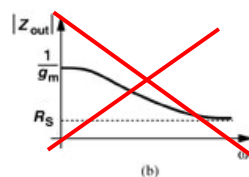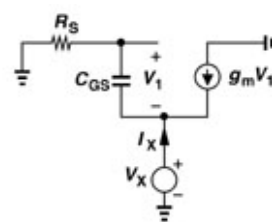- Increasing impedance with frequency  $\rightarrow$  inductive component!



(b)


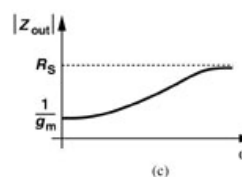


(c)

28
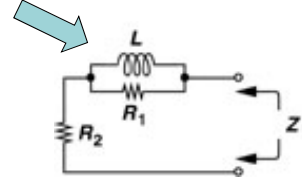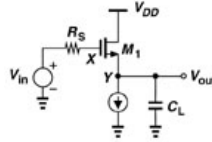
# SF Inductive component

- Assuming inductor
  - Replace with passive inductor equivalent




- Giving  $R_2 = 1/g_m$
- $R_1 = R_S - 1/g_m$

- Finding L

$$L \parallel R_1 \Rightarrow Z_{out} - 1/g_m = \frac{sR_S C_{GS} + 1}{g_m + sC_{GS}} - 1/g_m = \frac{sC_{GS}(R_S - 1/g_m)}{g_m + sC_{GS}}$$

- Conductance

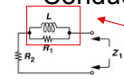

$$\frac{1}{Z_{out} - 1/g_m} = \frac{1}{R_S - 1/g_m} + \frac{1}{s \frac{C_{GS}}{g_m} (R_S - 1/g_m)}$$

$$\Rightarrow L = \frac{C_{GS}}{g_m} (R_S - 1/g_m)$$


Inductive property dependant on  $R_S$

29

TSL inf3410

# Source follower instability

- For large  $R_S$

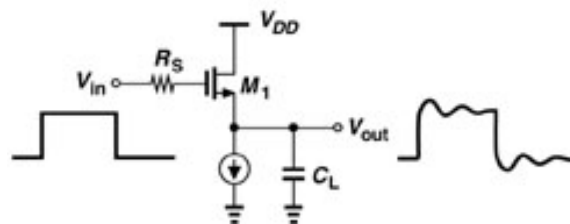

- Ringing on signal
  - Should be avoided

30


TSL inf3410
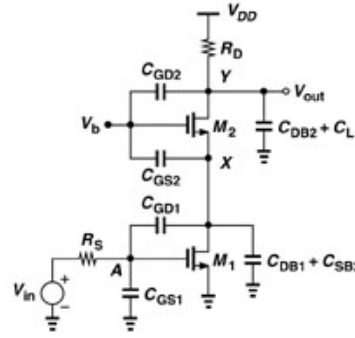
# Cascode stage frequency response



- Cascode

- Cascaded CS+CG
- High gain of CS
  - High impedance input
- High speed of CG
  - Suppressing Miller effect



- Node capacitances

- Node A:  $C_{GS1}$  to gnd and  $C_{GD1}$
- Node X:  $C_{DB1} + C_{SB2} + C_{GS2}$
- Node Y:  $C_{GD2} + C_{DB2} + C_L$

- Gain  $A \rightarrow X$ :  $A = G_m R_{out} = -g_{m1} \frac{1}{g_{m2} + g_{mb2}} \approx 1$

- Assuming similar size

- Miller cap:  $(1 + A)C_{GD1} \approx 2C_{GD1}$  *Ignorable Miller capacitance*

31

# Cascode poles



- Pole in node A

$$\omega_{p,A} = \frac{1}{R_S \left[ C_{GS1} + \left( 1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]}$$


- Pole in node X

$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}}$$

- Pole in output node

$$\omega_{p,Y} = \frac{1}{R_D (C_{DB2} + C_L + C_{GD2})}$$

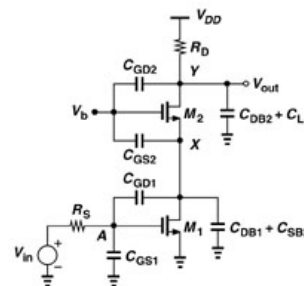- Pole in X are often moved upwards in frequency for stability




TSL inf3410

32

# Differential pair freq. response



- Analyze by half-circuit

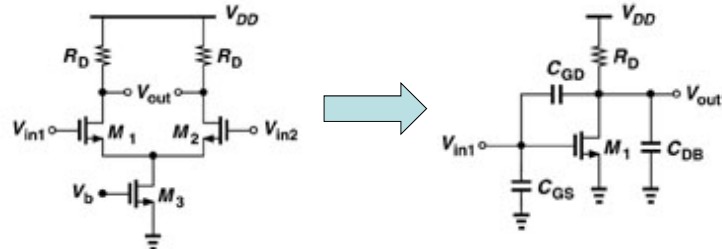

- Response identical to CS response
- Number of poles is symmetrical
  - Analyze poles of half-circuit


TSL inf3410

33
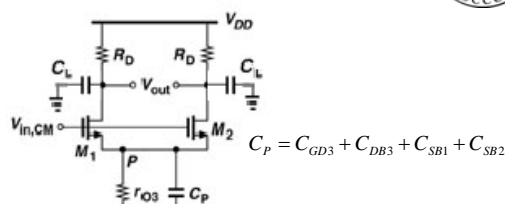
# Differential pair CM freq. response



- Common-mode
  - M<sub>1</sub> – M<sub>3</sub> large devices
  - Substantial load at P
- Common-mode to differential error



$$A_{V,CM-DM}(s) = \frac{V_X - V_Y}{V_{in,CM}} = - \frac{(g_{m1} - g_{m2})[R_D \parallel \frac{1}{C_L s}]}{(g_{m1} + g_{m2})[r_{o3} \parallel \frac{1}{C_P s}] + 1} = - \frac{(g_{m1} - g_{m2})R_D}{(g_{m1} + g_{m2})r_{o3} + 1} \cdot \frac{(1 + s r_{o3} C_P)}{(1 + s R_D C_L)(1 + s \frac{r_{o3} C_P}{(g_{m1} + g_{m2})r_{o3} + 1})}$$

$$A_{CM-DM} = \frac{V_X - V_Y}{V_{in,CM}} = - \frac{(g_{m1} - g_{m2})R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$

$R_D \rightarrow R_D \parallel \frac{1}{C_L s}$      $R_{SS} \rightarrow r_{o3} \parallel \frac{1}{C_P s}$

- Due to input device mismatch
- Output pole  $\gg$  pole at P  $\rightarrow$  poor CMRR
- Zero dominates

TSL inf3410


$A_{CM-DM}$  raising  $\omega > \frac{1}{r_{o3} C_P}$  34



# Diff-pair poles


- P poles  $\ll$  output poles

- Poor CMRR

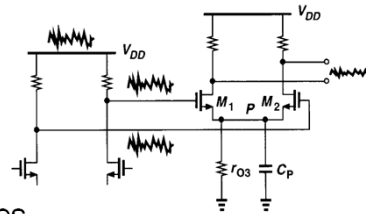

- Often due to large devices

- Maintain headroom

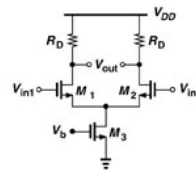

TSL inf3410


35


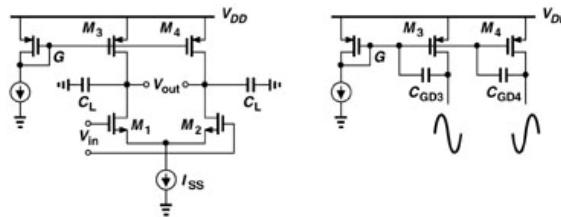
# Diff-pair with high-impedance load

- Analyzing differential and CM separately

- $C_L$  includes  $C_{GD}$  and  $C_{DB}$  of PMOS loads



- For differential outputs,  $C_{GD3}$  and  $C_{GD4}$  conduct equal and opposite currents to node G
  - Therefore node G is ground for small-signal analysis
  - In practice: We hook up by-pass capacitor between G and ground


TSL inf3410

36



# Half-circuit analysis

- Using previous analysis

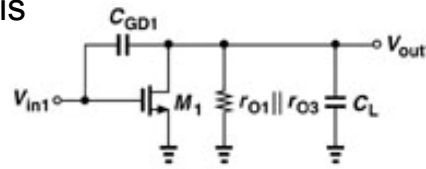

$$R_D \rightarrow r_{o1} \parallel r_{o3}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(sC_{GD} - g_m)R_D}{s^2 R_S R_D (C_{GS} C_{GD} + C_{GS} C_{SB} + C_{GD} C_L) + s[R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_L)] + 1}$$

Eq 6.23

- Dominant pole

$$\frac{1}{(r_{o1} \parallel r_{o3})C_L}$$


TSL inf3410

37

# Diff pair with active load



- Poles in two signal paths

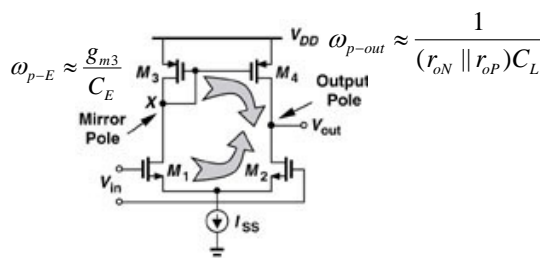



$$\omega_{p-E} \approx \frac{g_{m3}}{C_E} \quad \omega_{p-out} \approx \frac{1}{(r_{oN} \parallel r_{oP})C_L}$$

- Frequency response

$$V_E = (V_{out} - V_X) \frac{\frac{1}{sC_E + g_{mP}}}{\frac{1}{sC_E + g_{mP}} + R_X}$$

Assuming:  $g_{mP} \ll r_{OP}$

TSL inf3410

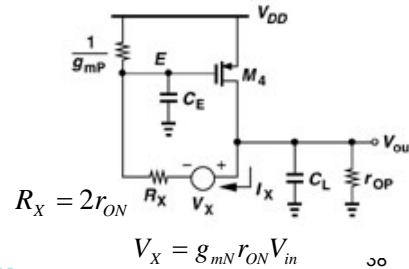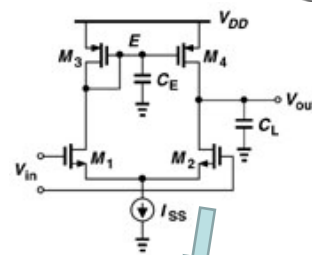


$$R_X = 2r_{ON}$$

$$V_X = g_{mN} r_{ON} V_{in} \quad \infty$$



- Using KCL
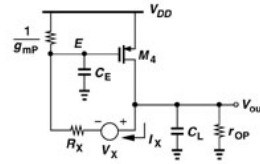
$$V_{out}(sC_L + r_{OP}^{-1}) + g_{m4}V_E + I_X = 0$$



$$\frac{V_{out}}{V_{in}} = \frac{g_{mN}r_{ON}(2g_{mP} + sC_E)}{s^2(2r_{OP}r_{ON}C_EC_L) + s[(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L] + 2g_{mP}(r_{ON} + r_{OP})}$$

- Mirror pole often higher in magnitude

$$\omega_{p-out} \approx \frac{2g_{mP}(r_{ON} + r_{OP})}{[(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L]} \approx \frac{1}{(r_{ON} \parallel r_{OP})C_L}$$


– Neglecting first term in denominator

– And  $2g_{mP}r_{ON} \gg 1$

- Zero

– Due to slow+fast signal path  $\omega_Z = \frac{2g_{mP}}{C_E}$
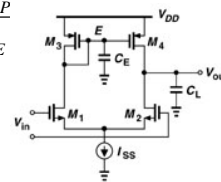
$$\omega_{p-E} \approx \frac{g_{mP}}{C_E}$$



TSL inf3410



- Classic transfer function (2. order)

- Determine stability
- $\omega_0$  -- pole frequency
- Q – Quality factor

$$A(s) = A(0) \frac{N(s)}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

$$Q < \sqrt{1/2} = 0.707$$

- Unconditionally stable
- Max magnitude at DC

$$Q = \sqrt{1/2}$$

- -3db frequency is  $\omega_0$

$$Q > 0.5$$

- Ringing overshoot

$$\% overshoot = 100e^{-\pi\sqrt{4Q^2-1}}$$

- No overshoot (only real poles)

$$Q < 0.5$$

TSL inf3410

40